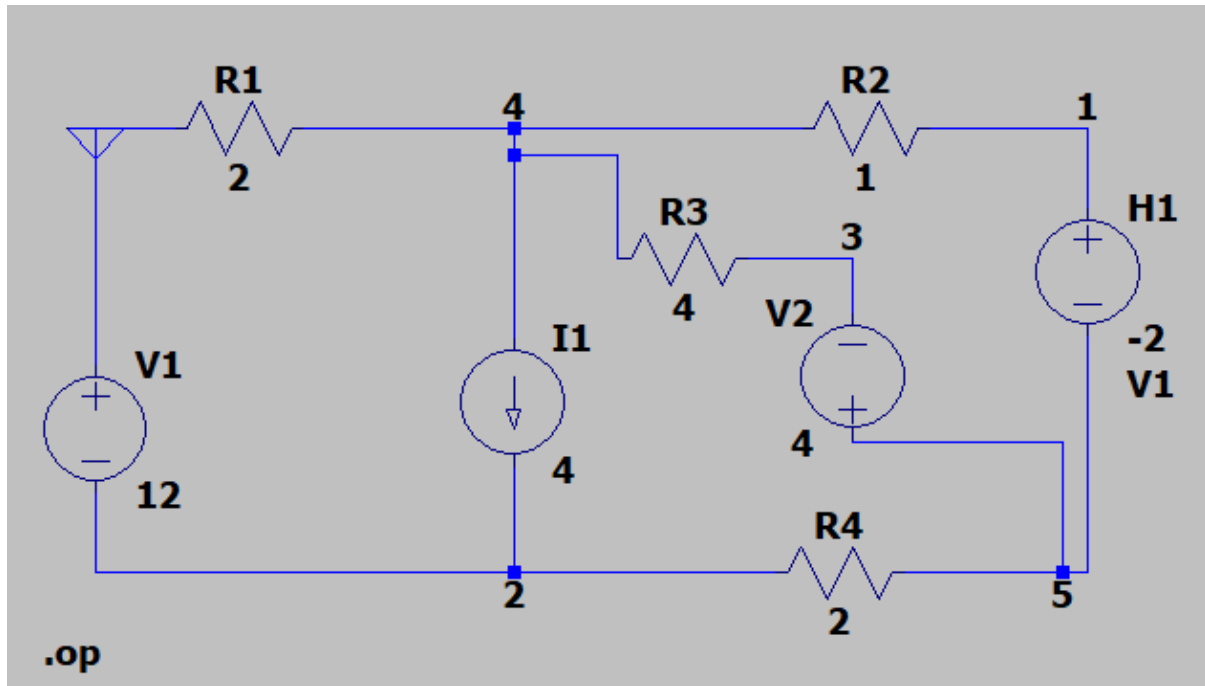



Referat lucrare de laborator 2 – Constantinescu Vlad 314CB

Exercitiu a)




```
--- Operating Point ---  
V(4) :          -7.5          voltage  
V(1) :          -5           voltage  
V(5) :         -12.5         voltage  
V(2) :          -12          voltage  
V(3) :         -16.5         voltage  
I(H1) :          -2.5         device_current  
I(I1) :           4           device_current  
I(R3) :         -2.25         device_current  
I(R4) :         -0.25         device_current  
I(R2) :           2.5         device_current  
I(R1) :         -3.75         device_current  
I(V2) :         -2.25         device_current  
I(V1) :         -3.75         device_current
```

Exercitiul b)

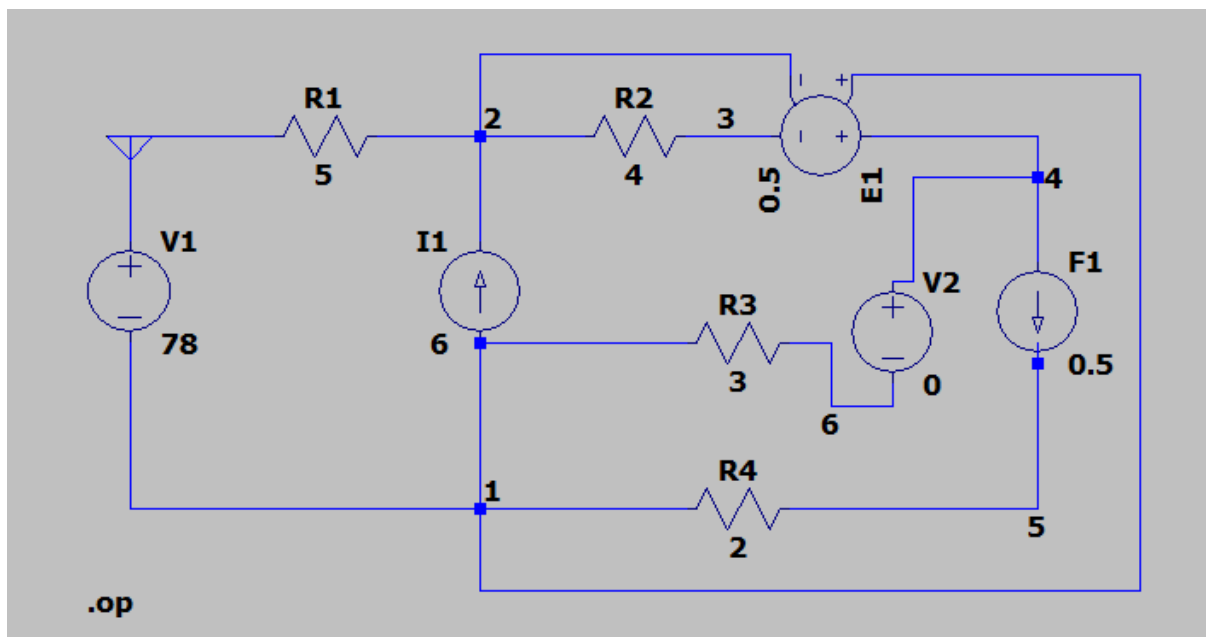

V(2) :	-1.76471	voltage
V(3) :	-27.1765	voltage
V(6) :	-65.2941	voltage
V(1) :	-78	voltage
V(5) :	-73.7647	voltage
V(4) :	-65.2941	voltage
I (F1) :	2.11765	device_current
I (I1) :	6	device_current
I (R4) :	2.11765	device_current
I (R3) :	4.23529	device_current
I (R2) :	-6.35294	device_current
I (R1) :	-0.352941	device_current
I (E1) :	-6.35294	device_current
I (V2) :	4.23529	device_current
I (V1) :	-0.352941	device_current

Exercitiul c)

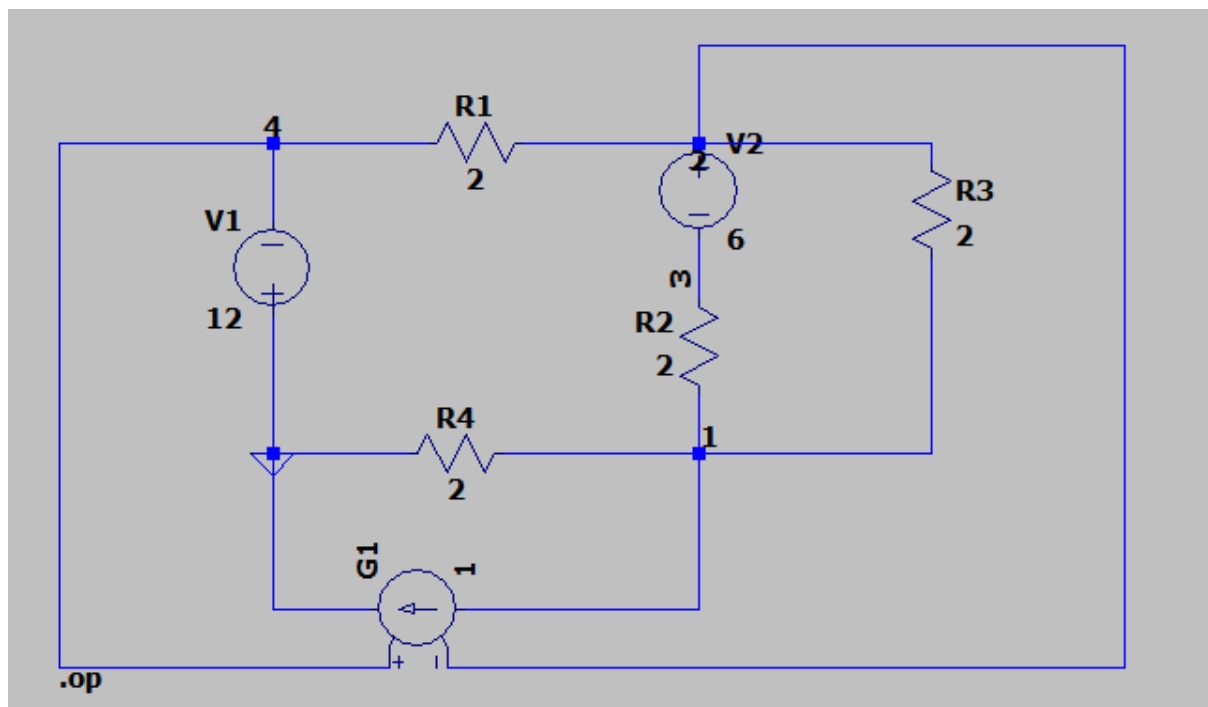

```

--- Operating Point ---
V(2):          18          voltage
V(4):          -12         voltage
V(1):           30         voltage
V(3):           12         voltage
I(R4):          15         device_current
I(R3):          -6         device_current
I(R2):           9         device_current
I(R1):          15         device_current
I(G1):         -30         device_current
I(V2):          -9         device_current
I(V1):         -15         device_current

```