

Digital Logic & Computer Design

CS 4341

Professor Dan Moldovan
Spring 2010

Chapter 5 :: Digital Building Blocks

Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris

Chapter 5 :: Topics


- **Introduction**
- **Arithmetic Circuits**
- **Number Systems**
- **Sequential Building Blocks**
- **Memory Arrays**
- **Logic Arrays**

Introduction

- Digital building blocks:
 - Gates, multiplexers, decoders, registers, arithmetic circuits, counters, memory arrays, logic arrays
- Building blocks demonstrate hierarchy, modularity, and regularity:
 - Hierarchy of simpler components
 - Well-defined interfaces and functions
 - Regular structure easily extended to different sizes
- Will use many of these building blocks to build a microprocessor in Chapter 7

1-Bit Adders

Half Adder

 


A	B	C _{out}	S
0	0		
0	1		
1	0		
1	1		

$$S =$$

$$C_{out} =$$

Full Adder

 


C _{in}	A	B	C _{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$$S =$$

$$C_{out} =$$

1-Bit Adders

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S =$$

$$C_{out} =$$

Full Adder

 


C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S =$$

$$C_{out} =$$

1-Bit Adders

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

 

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Multibit Adder, also called CPA


- Several types of carry propagate adders (CPAs) are:
 - Ripple-carry adders (slow)
 - Carry-lookahead adders (fast)
 - Prefix adders (faster)
- Carry-lookahead and prefix adders are faster for large adders but require more hardware.

Symbol

 

Ripple-Carry Adder

 - Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



Ripple-Carry Adder Delay

- The delay of an N -bit ripple-carry adder is:

$$t_{\text{ripple}} = Nt_{FA}$$

where t_{FA} is the delay of a full adder

Carry-Lookahead Adder

- Compute carry out (C_{out}) for k -bit blocks using *generate* and *propagate* signals
- **Some definitions:**
 - A column (bit i) produces a carry out by either *generating* a carry out or *propagating* a carry in to the carry out.
 - Generate (G_i) and propagate (P_i) signals for each column:
 - A column will generate a carry out if A_i AND B_i are both 1.

$$G_i = A_i B_i$$

- A column will propagate a carry in to the carry out if A_i OR B_i is 1.

$$P_i = A_i + B_i$$

- The carry out of a column (C_i) is:

$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$$

Carry-Lookahead Addition

- Step 1: compute *generate* (G) and *propagate* (P) signals for columns (single bits)
- Step 2: compute G and P for k -bit blocks
- Step 3: C_{in} propagates through each k -bit propagate/generate block

Carry-Lookahead Adder

- For example, we can calculate generate and propagate signals for a 4-bit block ($G_{3:0}$ and $P_{3:0}$) :
 - A 4-bit block will generate a carry out if column 3 generates a carry (G_3) or if column 3 propagates a carry (P_3) that was generated or propagated in a previous column as described by the following equation:

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$


- A 4-bit block will propagate a carry in to the carry out if all of the columns propagate the carry:

$$P_{3:0} = P_3 P_2 P_1 P_0$$

- The carry out of the 4-bit block (C_i) is:

$$C_i = G_{i:j} + P_{i:j} C_{j-1}$$

32-bit CLA with 4-bit blocks

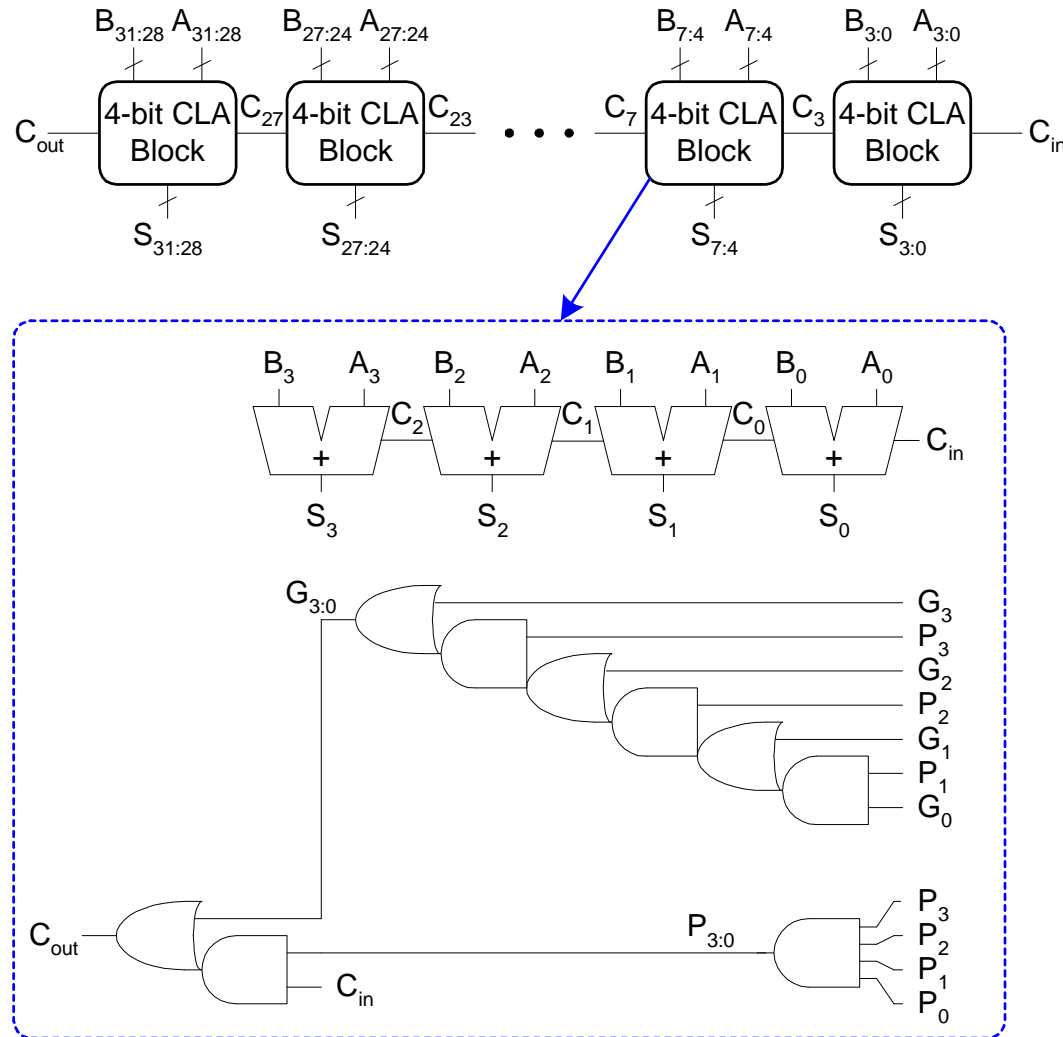

Carry-Lookahead Adder Delay

- Delay of an N -bit carry-lookahead adder with k -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA}$$

where

- t_{pg} : delay of the column generate and propagate gates
 - t_{pg_block} : delay of the block generate and propagate gates
 - t_{AND_OR} : delay from C_{in} to C_{out} of the final AND/OR gate in the k -bit CLA block
- An N -bit carry-lookahead adder is generally much faster than a ripple-carry adder for $N > 16$

Prefix Adder

- Computes the carry in (C_{i-1}) for each of the columns as fast as possible and then computes the sum:

$$S_i = (A_i \oplus B_i) \oplus C_i$$

- Computes G and P for 1-bit, then 2-bit blocks, then 4-bit blocks, then 8-bit blocks, etc. until the carry in (generate signal) is known for each column
- Has $\log_2 N$ stages

Prefix Adder

- A carry in is produced by being either *generated* in a column or *propagated* from a previous column.
- Define column -1 to hold C_{in} , so
- Then, the carry in to column i = the carry out of column $i-1$:

$$G_{-1} = C_{in}, P_{-1} = 0$$

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$ is the generate signal spanning columns $i-1$ to -1.

There will be a carry out of column $i-1$ (C_{i-1}) if the block spanning columns $i-1$ through -1 generates a carry.

- Thus, we can rewrite the sum equation as:

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

- **Goal:** Quickly compute $G_{0:-1}$, $G_{1:-1}$, $G_{2:-1}$, $G_{3:-1}$, $G_{4:-1}$, $G_{5:-1}$,
(These are called the *prefixes*)

Prefix Adder


- The generate and propagate signals for a block spanning bits $i:j$ are:

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$




$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- In words, these prefixes describe that:
 - A block will generate a carry if the upper part ($i:k$) generates a carry or if the upper part propagates a carry generated in the lower part ($k-1:j$)
 - A block will propagate a carry if both the upper and lower parts propagate the carry.

Prefix Adder Schematic

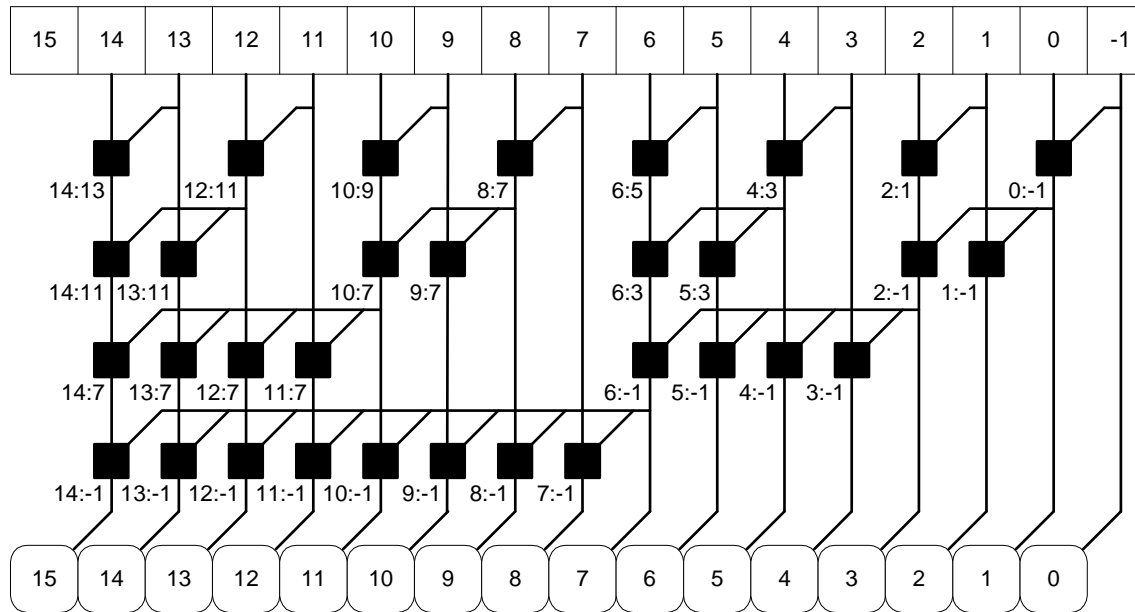

Legend

   

Prefix Adder Delay

- The delay of an N -bit prefix adder is:

$$t_{PA} = t_{pg} + \log_2 N (t_{pg_prefix}) + t_{XOR}$$

where

- t_{pg} is the delay of the column generate and propagate gates (AND or OR gate)
- t_{pg_prefix} is the delay of the black prefix cell (AND-OR gate)

Adder Delay Comparisons

- Compare the delay of 32-bit ripple-carry, carry-lookahead, and prefix adders. The carry-lookahead adder has 4-bit blocks. Assume that each two-input gate delay is 100 ps and the full adder delay is 300 ps.

Adder Delay Comparisons

- Compare the delay of 32-bit ripple-carry, carry-lookahead, and prefix adders. The carry-lookahead adder has 4-bit blocks. Assume that each two-input gate delay is 100 ps and the full adder delay is 300 ps.


$$\begin{aligned}t_{\text{ripple}} &= Nt_{FA} = 32(300 \text{ ps}) \\ &= 9.6 \text{ ns}\end{aligned}$$

$$\begin{aligned}t_{CLA} &= t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA} \\ &= [100 + 600 + (7)200 + 4(300)] \text{ ps} \\ &= 3.3 \text{ ns}\end{aligned}$$


$$\begin{aligned}t_{PA} &= t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR} \\ &= [100 + \log_2 32(200) + 100] \text{ ps} \\ &= 1.2 \text{ ns}\end{aligned}$$

Subtractor

Symbol

 


Implementation

 


Comparator: Equality

Symbol

 


Implementation

 


Comparator: Less Than

- For unsigned numbers

 


Arithmetic Logic Unit (ALU)

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT


ALU Design

 


$F_{2:0}$	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & $\sim B$
101	A $\sim B$
110	A - B
111	SLT

Set Less Than (SLT) Example

 - Configure a 32-bit ALU for the set if less than (SLT) operation. Suppose $A = 25$ and $B = 32$.



Set Less Than (SLT) Example

 

- Configure a 32-bit ALU for the set if less than (SLT) operation. Suppose $A = 25$ and $B = 32$.
 - A is less than B , so we expect Y to be the 32-bit representation of 1 (0x00000001).
 - For SLT, $F_{2:0} = 111$.
 - $F_2 = 1$ configures the adder unit as a subtracter. So $25 - 32 = -7$.
 - The two's complement representation of -7 has a 1 in the most significant bit, so $S_{31} = 1$.
 - With $F_{1:0} = 11$, the final multiplexer selects $Y = S_{31}$ (zero extended) = 0x00000001.



Shifters

- **Logical shifter:** shifts value to left or right and fills empty spaces with 0's
 - Ex: 11001 >> 2 =
 - Ex: 11001 << 2 =
- **Arithmetic shifter:** same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb).
 - Ex: 11001 >>> 2 =
 - Ex: 11001 <<< 2 =
- **Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end
 - Ex: 11001 ROR 2 =
 - Ex: 11001 ROL 2 =

Shifters

- **Logical shifter:** shifts value to left or right and fills empty spaces with 0's
 - Ex: $11001 \gg 2 = 00110$
 - Ex: $11001 \ll 2 = 00100$
- **Arithmetic shifter:** same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb).
 - Ex: $11001 \ggg 2 = 11110$
 - Ex: $11001 \lll 2 = 00100$
- **Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end
 - Ex: $11001 \text{ ROR } 2 = 01110$
 - Ex: $11001 \text{ ROL } 2 = 00111$

Shifter Design

  

Shifters as Multipliers and Dividers

- A left shift by N bits multiplies a number by 2^N
 - Ex: $00001 \ll 2 = 00100$ ($1 \times 2^2 = 4$)
 - Ex: $11101 \ll 2 = 10100$ ($-3 \times 2^2 = -12$)
- The arithmetic right shift by N divides a number by 2^N
 - Ex: $01000 \ggg 2 = 00010$ ($8 \div 2^2 = 2$)
 - Ex: $10000 \ggg 2 = 11100$ ($-16 \div 2^2 = -4$)

Multipliers

- Steps of multiplication for both decimal and binary numbers:
 - Partial products are formed by multiplying a single digit of the multiplier with the entire multiplicand
 - Shifted partial products are summed to form the result

Decimal

$$\begin{array}{r} 230 \\ \times 42 \\ \hline 460 \\ + 920 \\ \hline 9660 \end{array}$$

multiplicand

multiplier

partial
products

result


$$230 \times 42 = 9660$$

Binary


$$\begin{array}{r} 0101 \\ \times 0111 \\ \hline 0101 \\ 0101 \\ 0101 \\ + 0000 \\ \hline 0100011 \end{array}$$

$$5 \times 7 = 35$$

4 x 4 Multiplier

 
 
$$\begin{array}{r}
 \begin{array}{cccc}
 & A_3 & A_2 & A_1 & A_0 \\
 \times & B_3 & B_2 & B_1 & B_0 \\
 \hline
 & A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \\
 A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 & \\
 A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 & \\
 + & A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$



Division Algorithm

- $Q = A/B$
- R : remainder
- D : difference

$$R = A$$

for $i = N-1$ to 0


$$D = R - B$$

if $D < 0$ then $Q_i = 0, R' = R$ // $R < B$

else $Q_i = 1, R' = D$ // $R \geq B$

$$R = 2R'$$

4 x 4 Divider

 

Copy

© 2007 Elsevier, Inc. All rights reserved

Number Systems

- What kind of numbers do you know how to represent using binary representations?
 - Positive numbers
 - Unsigned binary
 - Negative numbers
 - Two's complement
 - Sign/magnitude numbers
- What about fractions?

Numbers with Fractions

- Two common notations:
 - Fixed-point:
the binary point is fixed
 - Floating-point:
the binary point floats to the right of the most significant 1

Fixed-Point Numbers

- Fixed-point representation of 6.75 using 4 integer bits and 4 fraction bits:

01101100

0110.1100

$$2^2 + 2^1 + 2^{-1} + 2^{-2} = 6.75$$

- The binary point is not a part of the representation but is implied.
- The number of integer and fraction bits must be agreed upon by those generating and those reading the number.

Fixed-Point Numbers

- Ex: Represent 7.5_{10} using an 8-bit binary representation with 4 integer bits and 4 fraction bits.

Fixed-Point Numbers

- Ex: Represent 7.5_{10} using an 8-bit binary representation with 4 integer bits and 4 fraction bits.

01111000

Signed Fixed-Point Numbers

- As with integers, negative fractional numbers can be represented two ways:
 - Sign/magnitude notation
 - Two's complement notation
- Represent -7.5_{10} using an 8-bit binary representation with 4 integer bits and 4 fraction bits.
 - Sign/magnitude:
 - Two's complement:

Signed Fixed-Point Numbers

- As with integers, negative fractional numbers can be represented two ways:
 - Sign/magnitude notation
 - Two's complement notation
- Represent -7.5_{10} using an 8-bit binary representation with 4 integer bits and 4 fraction bits.
 - Sign/magnitude:
11111000
 - Two's complement:

Signed Fixed-Point Numbers

- As with integers, negative fractional numbers can be represented two ways:
 - Sign/magnitude notation
 - Two's complement notation
- Represent -7.5_{10} using an 8-bit binary representation with 4 integer bits and 4 fraction bits.

- Sign/magnitude:

11111000

- Two's complement:

1. +7.5: 01111000

2. Invert bits: 10000111

3. Add 1 to lsb:
$$\begin{array}{r} + \quad 1 \\ \hline 10001000 \end{array}$$

Floating-Point Numbers

- The binary point floats to the right of the most significant 1.
- Similar to decimal scientific notation.
- For example, write 273_{10} in scientific notation:

$$273 = 2.73 \times 10^2$$


- In general, a number is written in scientific notation as:

$$\pm M \times B^E$$

Where,

- M = mantissa
- B = base
- E = exponent
- In the example, $M = 2.73$, $B = 10$, and $E = 2$

Floating-Point Numbers

 

- **Example:** represent the value 228_{10} using a 32-bit floating point representation

We show three versions - final version is called the **IEEE 754 floating-point standard**


Floating-Point Representation 1

- Convert the decimal number to binary:
 - $228_{10} = 11100100_2 = 1.11001 \times 2^7$
- Fill in each field of the 32-bit number:
 - The sign bit is positive (0)
 - The 8 exponent bits represent the value 7
 - The remaining 23 bits are the mantissa

1 bit	8 bits	23 bits
0	00000111	11 1001 0000 0000 0000 0000
Sign	Exponent	Mantissa

Floating-Point Representation 2

 - First bit of the mantissa is always 1:
 - $228_{10} = 11100100_2 = 1.11001 \times 2^7$
- Thus, storing the most significant 1, also called the *implicit leading 1*, is redundant information.
- Instead, store just the fraction bits in the 23-bit field. The leading 1 is implied.




Floating-Point Representation 3

- *Biased exponent*: bias = 127 (01111111_2)

- Biased exponent = bias + exponent
- Exponent of 7 is stored as:

$$127 + 7 = 134 = 0x10000110_2$$

 - The **IEEE 754 32-bit floating-point representation** of 228_{10}




Floating-Point Example

- Write the value -58.25_{10} using the IEEE 754 32-bit floating-point standard.

Floating-Point Example

 - Write the value -58.25_{10} using the IEEE 754 32-bit floating-point standard.
- Convert the decimal number to binary:
 - $58.25_{10} =$
- Fill in each field in the 32-bit number:
 - Sign bit:
 - 8 Exponent bits:
 - 23 fraction bits:



- In hexadecimal:

Floating-Point Example

- Write the value -58.25_{10} using the IEEE 754 32-bit floating-point standard.
- First, convert the decimal number to binary:
 - $58.25_{10} = 111010.01_2 = 1.1101001 \times 2^5$
- Next, fill in each field in the 32-bit number:
 - Sign bit: 1 (negative)
 - 8 exponent bits: $(127 + 5) = 132 = 10000100_2$
 - 23 fraction bits: 110 1001 0000 0000 0000 0000

1 bit	8 bits	23 bits
1	100 0010 0	110 1001 0000 0000 0000 0000
Sign	Exponent	Fraction

- In hexadecimal: 0xC2690000

Floating-Point Numbers: Special Cases

- The IEEE 754 standard includes special cases for numbers that are difficult to represent, such as 0 because it lacks an implicit leading 1.

Number	Sign	Exponent	Fraction
0	X	00000000	0000000000000000000000000000
∞	0	11111111	0000000000000000000000000000
$-\infty$	1	11111111	0000000000000000000000000000
NaN	X	11111111	non-zero

NaN is used for numbers that don't exist, such as $\sqrt{-1}$ or $\log(-5)$.

Floating-Point Number Precision

- Single-Precision:
 - 32-bit notation
 - 1 sign bit, 8 exponent bits, 23 fraction bits
 - bias = 127
- Double-Precision:
 - 64-bit notation
 - 1 sign bit, 11 exponent bits, 52 fraction bits
 - bias = 1023

Floating-Point Numbers: Rounding

- Overflow: number is too large to be represented
- Underflow: number is too small to be represented
- Rounding modes:
 - Down
 - Up
 - Toward zero
 - To nearest
- **Example:** round 1.100101 (1.578125) so that it uses only 3 fraction bits.
 - Down: 1.100
 - Up: 1.101
 - Toward zero: 1.100
 - To nearest: 1.101 (1.625 is closer to 1.578125 than 1.5 is)

Floating-Point Addition

1. Extract exponent and fraction bits
2. Prepend leading 1 to form mantissa
3. Compare exponents
4. Shift smaller mantissa if necessary
5. Add mantissas
6. Normalize mantissa and adjust exponent if necessary
7. Round result
8. Assemble exponent and fraction back into floating-point format

Floating-Point Addition: Example

Add the following floating-point numbers:

0x3FC00000

0x40500000

Floating-Point Addition: Example

1. Extract exponent and fraction bits

1 bit	8 bits	23 bits
0	01111111	100 0000 0000 0000 0000 0000
Sign	Exponent	Fraction

1 bit	8 bits	23 bits
0	10000000	101 0000 0000 0000 0000 0000
Sign	Exponent	Fraction

For first number (N1): $S = 0, E = 127, F = .1$

For second number (N2): $S = 0, E = 128, F = .101$

2. Prepend leading 1 to form mantissa

N1: 1.1

N2: 1.101

Floating-Point Addition: Example

3. Compare exponents

$127 - 128 = -1$, so shift N1 right by 1 bit

4. Shift smaller mantissa if necessary

shift N1's mantissa: $1.1 \gg 1 = 0.11$ ($\times 2^1$)

5. Add mantissas

$$\begin{array}{r} 0.11 \times 2^1 \\ + 1.101 \times 2^1 \\ \hline 10.011 \times 2^1 \end{array}$$

Floating-Point Addition: Example

6. Normalize mantissa and adjust exponent if necessary

$$10.011 \times 2^1 = 1.0011 \times 2^2$$

7. Round result

No need (fits in 23 bits)

8. Assemble exponent and fraction back into floating-point format

$$S = 0, E = 2 + 127 = 129 = 10000001_2, F = 001100..$$


1 bit	8 bits	23 bits
0	10000001	001 1000 0000 0000 0000 0000
Sign	Exponent	Fraction

Written in hexadecimal: 0x40980000


Counters

- Increments on each clock edge.
- Used to cycle through numbers. For example,
 - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- Example uses:
 - Digital clock displays
 - Program counter: keeps track of current instruction executing

Symbol

 


Implementation

 


Shift Register

- Shift a new value in on each clock edge
- Shift a value out on each clock edge
- *Serial-to-parallel converter*: converts serial input (S_{in}) to parallel output ($Q_{0:N-1}$)

Symbol:

 


Implementation:

 


Shift Register with Parallel Load

 - When $Load = 1$, acts as a normal N -bit register
- When $Load = 0$, acts as a shift register
- Now can act as a *serial-to-parallel converter* (S_{in} to $Q_{0:N-1}$) or a *parallel-to-serial converter* ($D_{0:N-1}$ to S_{out})






Memory Arrays

 - Efficiently store large amounts of data
- Three common types:
 - Dynamic random access memory (DRAM)
 - Static random access memory (SRAM)
 - Read only memory (ROM)
- An M -bit data value can be read or written at each unique N -bit address.



Memory Arrays

   
- Two-dimensional array of bit cells
- Each bit cell stores one bit
- An array with N address bits and M data bits:
 - 2^N rows and M columns
 - **Depth:** number of rows (number of words)
 - **Width:** number of columns (size of word)
 - **Array size:** depth \times width = $2^N \times M$



Memory Array: Example


- $2^2 \times 3$ -bit array
- Number of words: 4
- Word size: 3-bits
- For example, the 3-bit word stored at address 10 is 100

Example:

 


Address	Data			
11	0	1	0	depth ↑ ↓
10	1	0	0	
01	1	1	0	
00	0	1	1	
	width ←→			


Memory Arrays

 


Memory Array Bit Cells

 


Example:

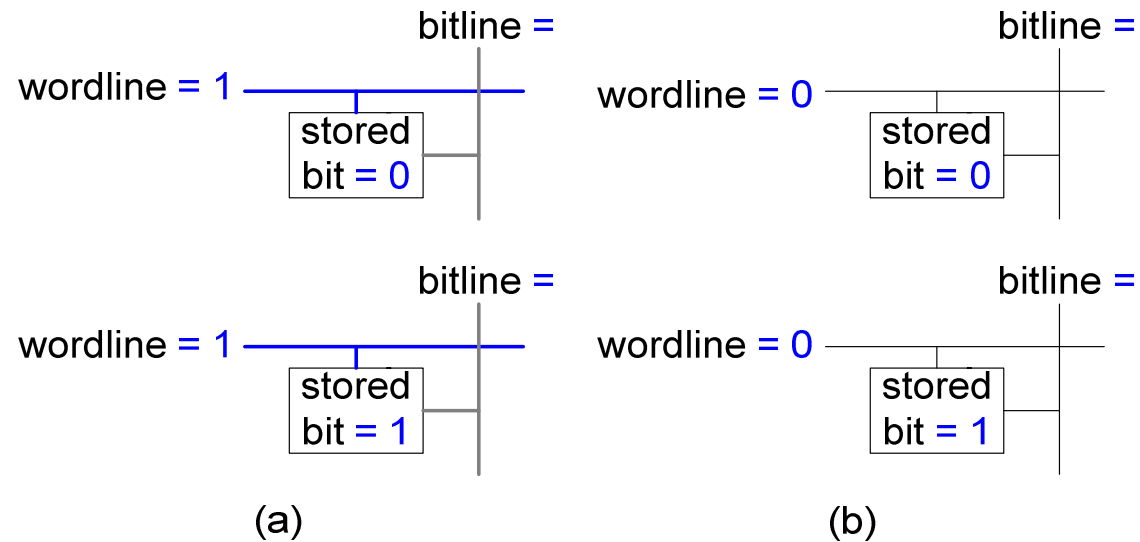

Memory Array Bit Cells

 


Example:

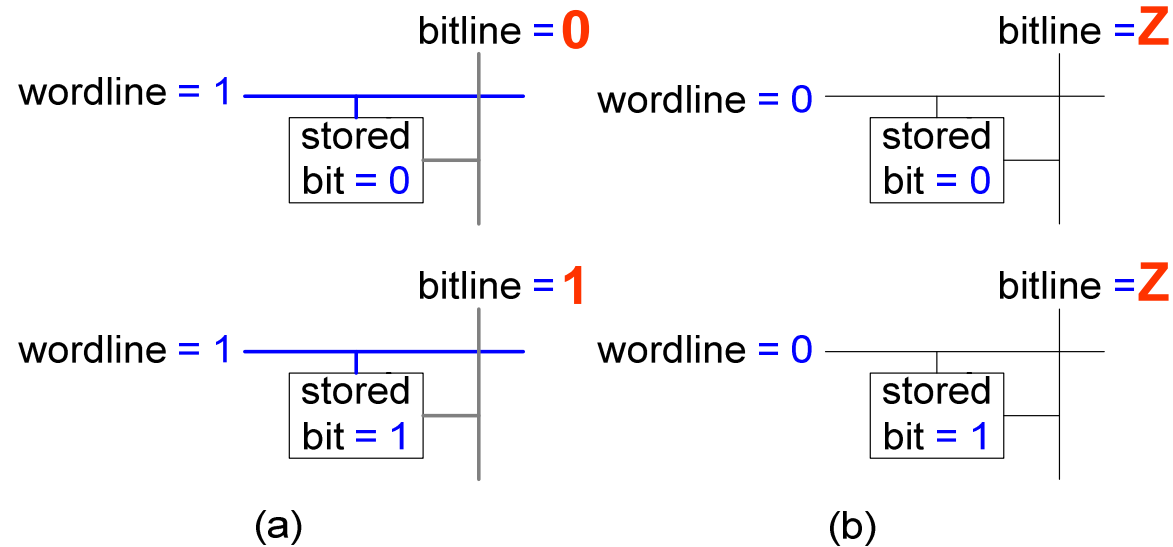

Memory Array

- **Wordline:**

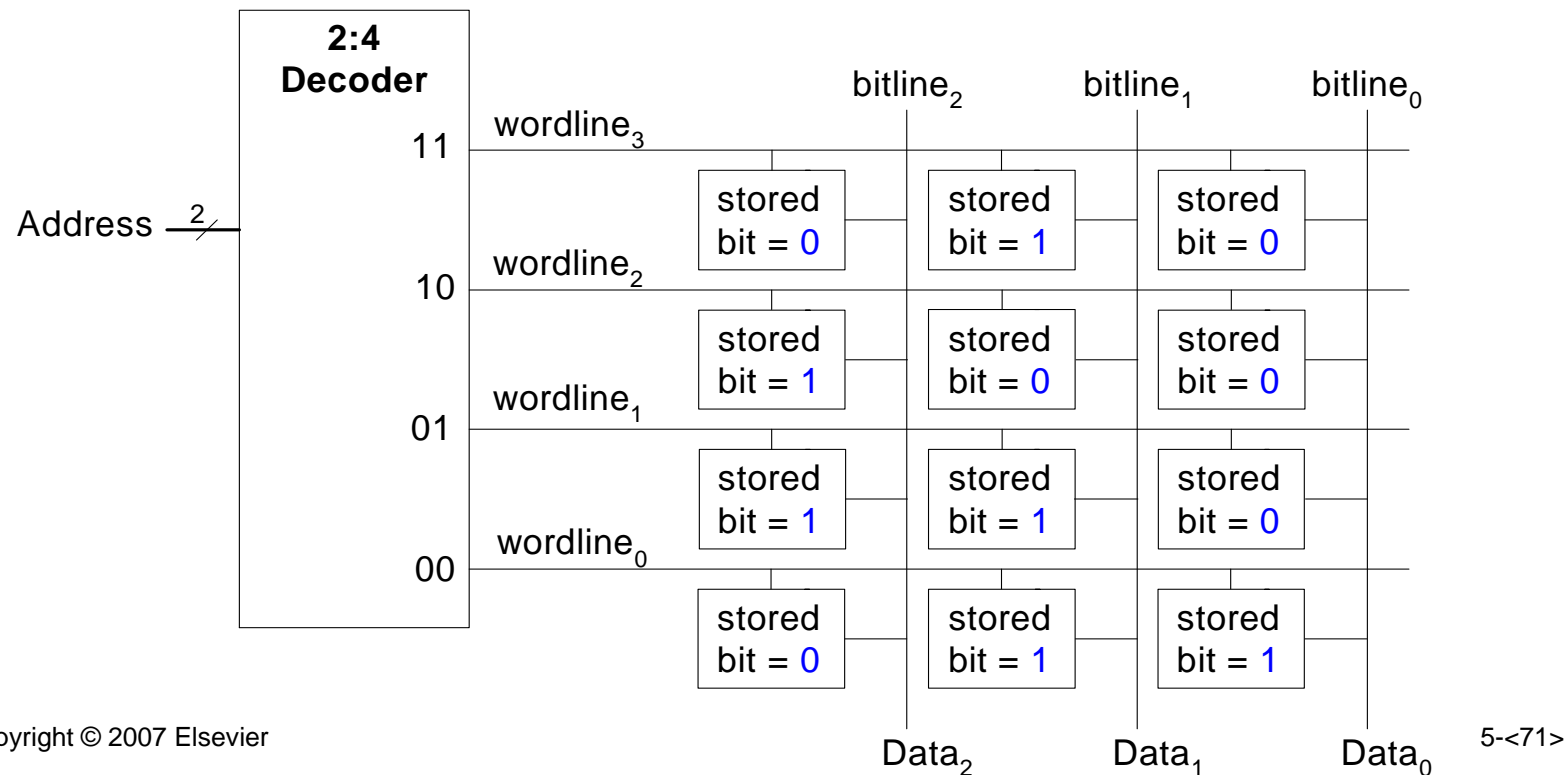- similar to an enable
- allows a single row in the memory array to be read or written
- corresponds to a unique address
- only one wordline is HIGH at any given time



Types of Memory

- Random access memory (RAM): **volatile**
- Read only memory (ROM): **nonvolatile**

RAM: Random Access Memory

- **Volatile:** loses its data when the power is turned off
- Read and written quickly
- Main memory in your computer is RAM (DRAM)

Historically called *random* access memory because any data word can be accessed as easily as any other (in contrast to sequential access memories such as a tape recorder)

ROM: Read Only Memory

- **Nonvolatile:** retains data when power is turned off
- Read quickly, but writing is impossible or slow
- Flash memory in cameras, thumb drives, and digital cameras are all ROMs

Historically called *read only* memory because ROMs were written at manufacturing time or by burning fuses. Once ROM was configured, it could not be written again. This is no longer the case for Flash memory and other types of ROMs.

Types of RAM

- Two main types of RAM:
 - Dynamic random access memory (DRAM)
 - Static random access memory (SRAM)
- Differ in how they store data:
 - DRAM uses a capacitor
 - SRAM uses cross-coupled inverters


Robert Dennard, 1932 -

- Invented DRAM in 1966 at IBM
- Others were skeptical that the idea would work
- By the mid-1970's DRAM was in virtually all computers





DRAM


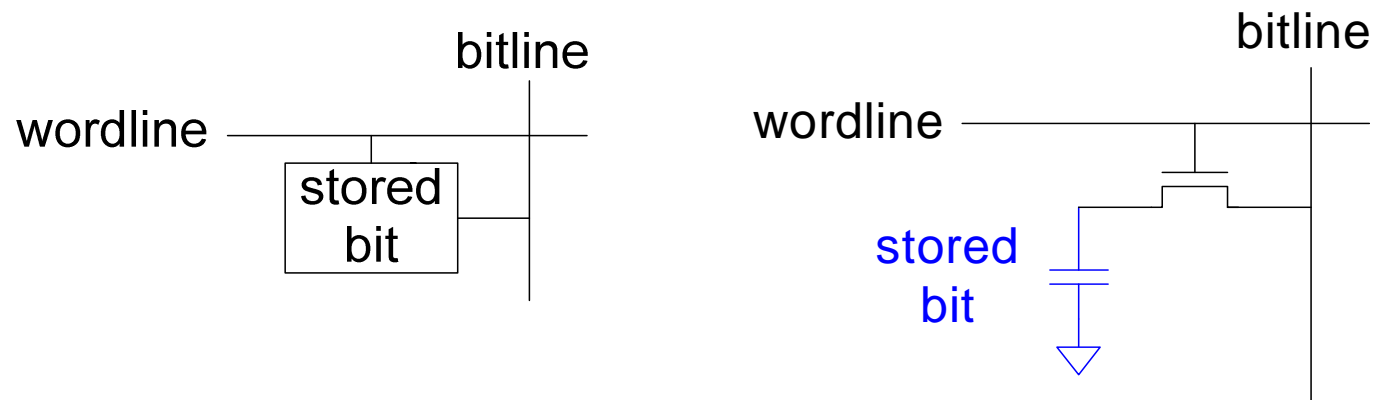
- Data bits stored on a capacitor
- Called *dynamic* because the value needs to be refreshed (rewritten) periodically and after being read:
 - Charge leakage from the capacitor degrades the value
 - Reading destroys the stored value




DRAM

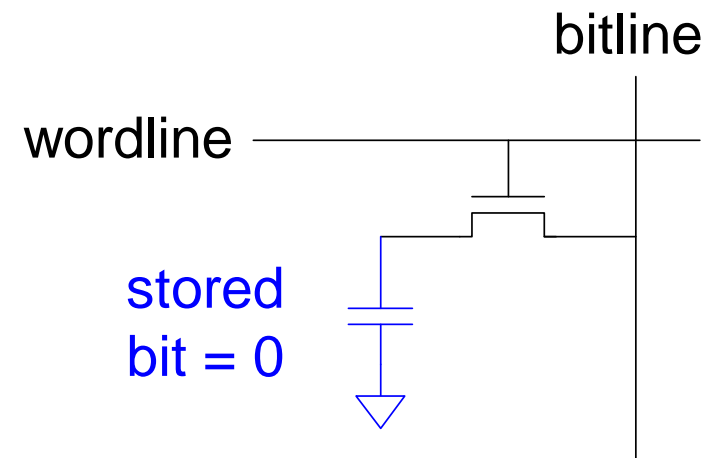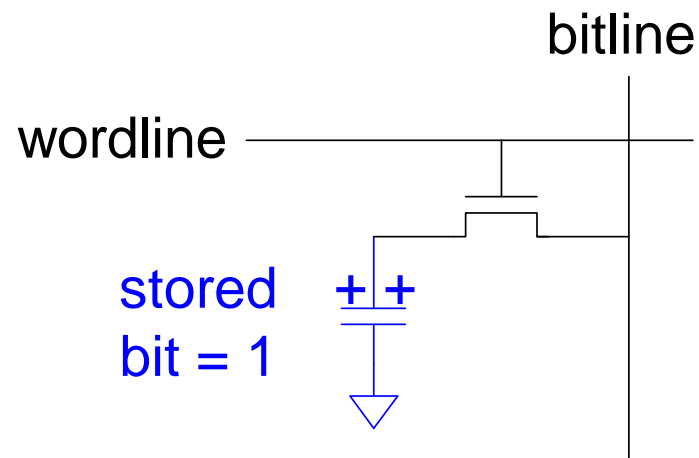


SRAM

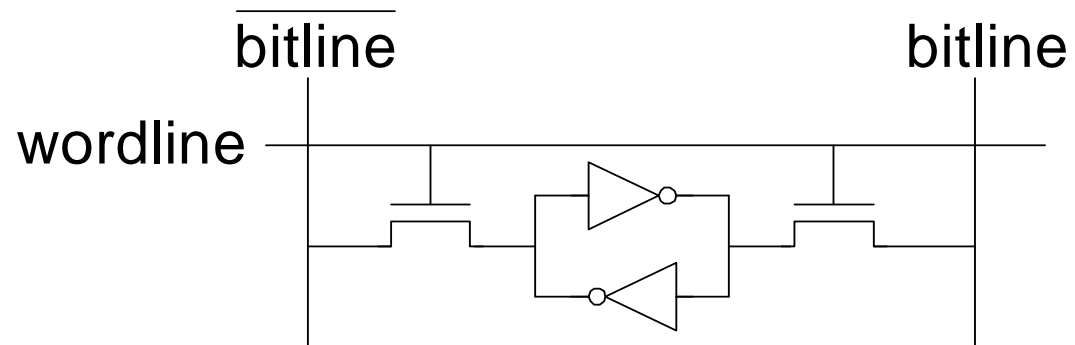 


Memory Arrays

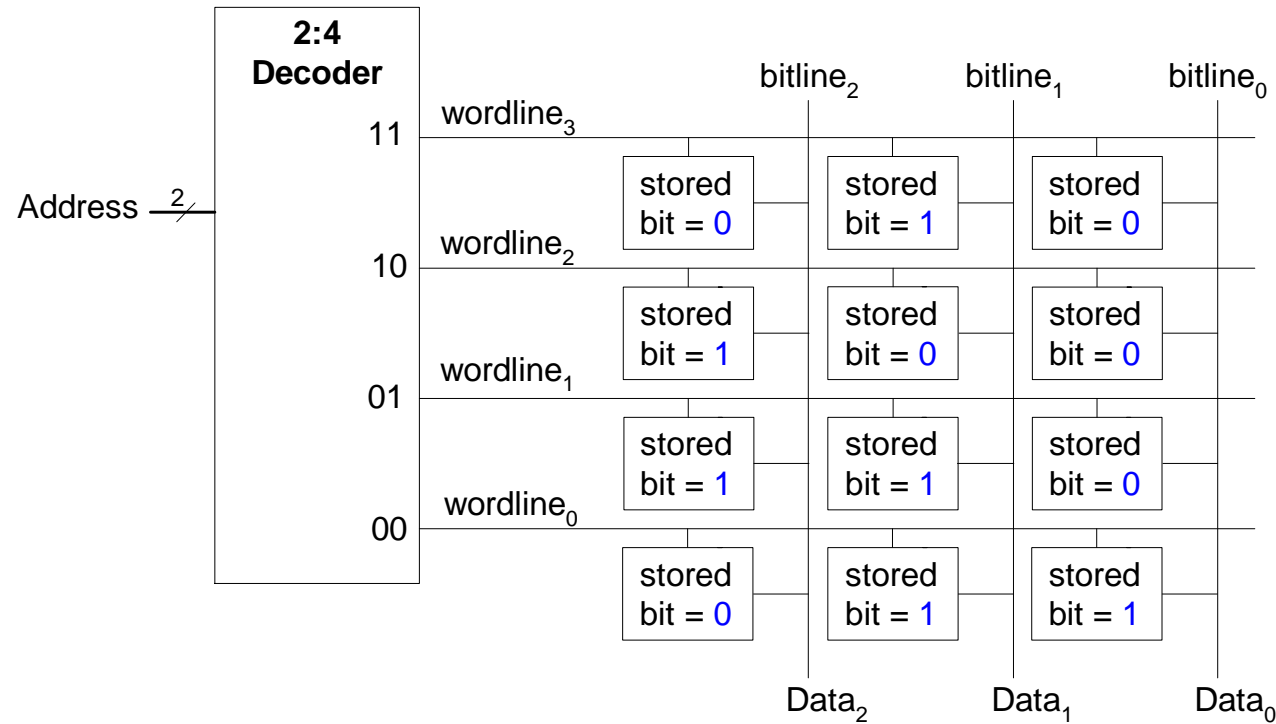



DRAM bit cell:

 

SRAM bit cell:

 

ROMs: Dot Notation

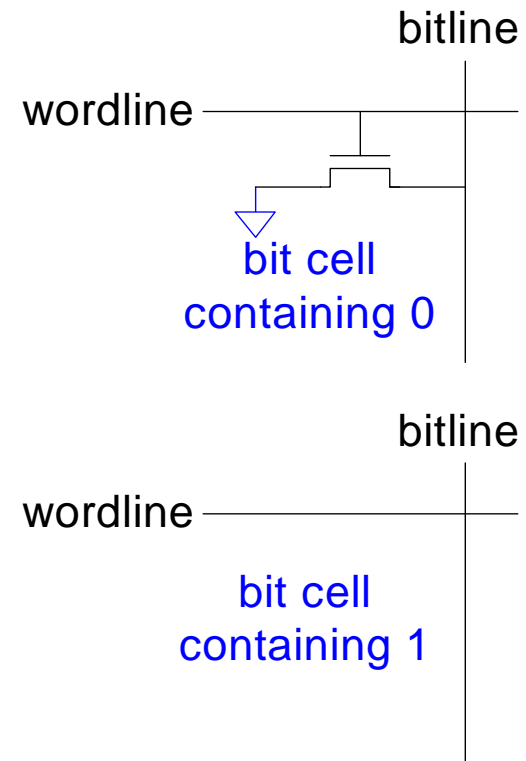 


Fujio Masuoka, 1944-

- Developed memories and high speed circuits at Toshiba from 1971-1994.
- Invented Flash memory as an unauthorized project pursued during nights and weekends in the late 1970's.
- The process of erasing the memory reminded him of the flash of a camera
- Toshiba slow to commercialize the idea; Intel was first to market in 1988
- Flash has grown into a \$25 billion per year market.




ROM Storage

 

Address	Data			depth ↑ ↓
11	0	1	0	
10	1	0	0	
01	1	1	0	
00	0	1	1	
width ←→				

ROM Logic

 


$$Data_2 = A_1 \oplus A_0$$

$$Data_1 = \overline{A_1} + A_0$$

$$Data_0 = \overline{A_1} \overline{A_0}$$

 
Example: Logic with ROMs

- Implement the following logic functions using a $2^2 \times 3$ -bit ROM:
 - $X = AB$
 - $Y = A + B$
 - $Z = \overline{AB}$




 Example: Logic with ROMs

- Implement the following logic functions using a $2^2 \times 3$ -bit ROM:
 - $X = AB$
 - $Y = A + B$
 - $Z = A \overline{B}$



Logic with Any Memory Array

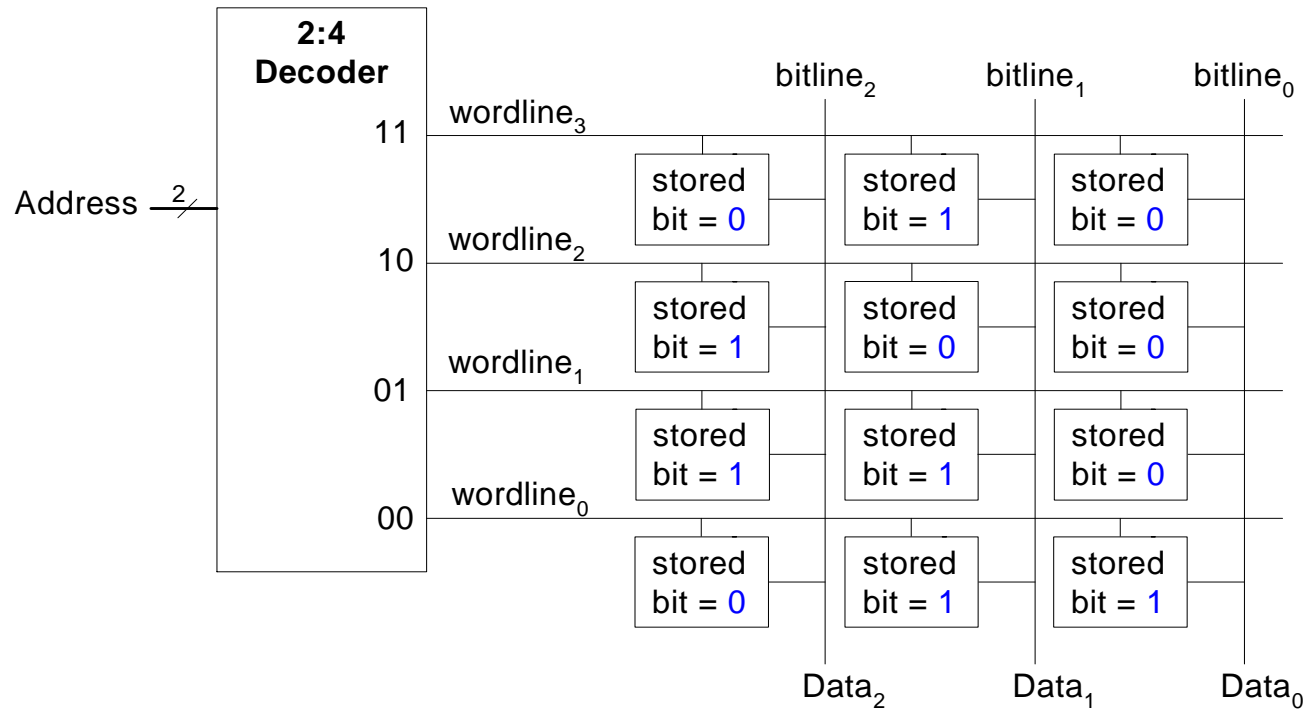


$$Data_2 = A_1 \oplus A_0$$

$$Data_1 = \overline{A_1} + A_0$$

$$Data_0 = \overline{A_1} \overline{A_0}$$

Logic with Memory Arrays

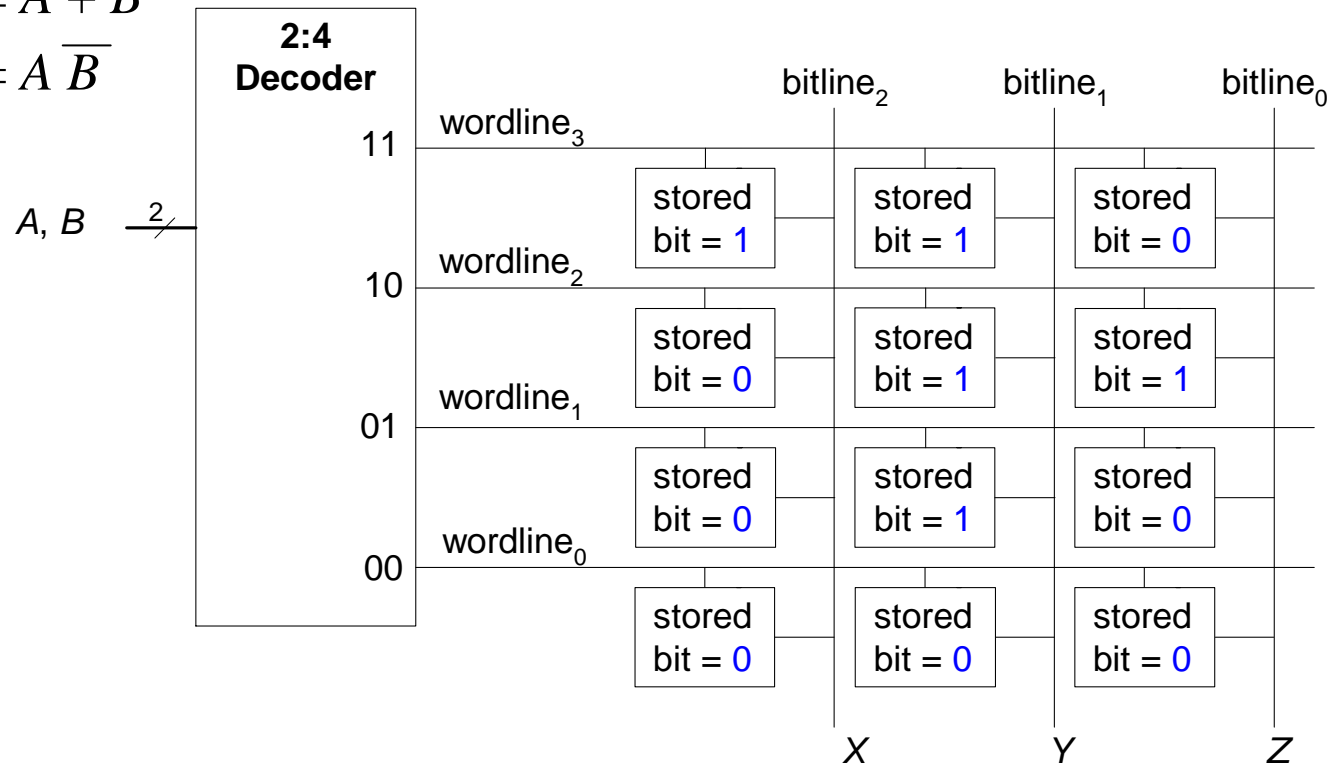
- Implement the following logic functions using a $2^2 \times 3$ -bit memory array:
 - $X = AB$
 - $Y = A + B$
 - $Z = A \overline{B}$



Logic with Memory Arrays


- Called *lookup tables* (LUTs): look up output at each input combination (address)

Truth Table		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

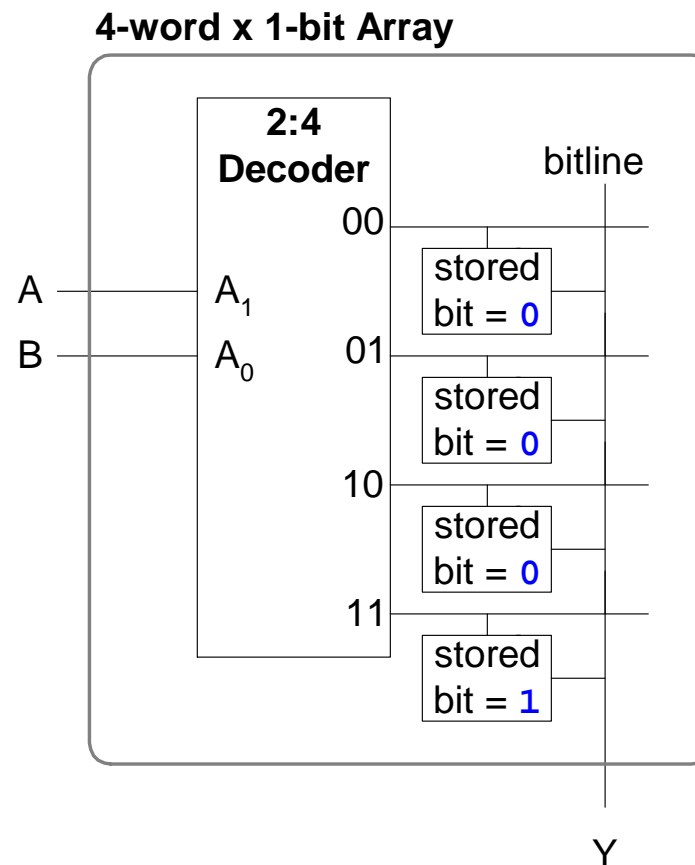

Multi-ported Memories

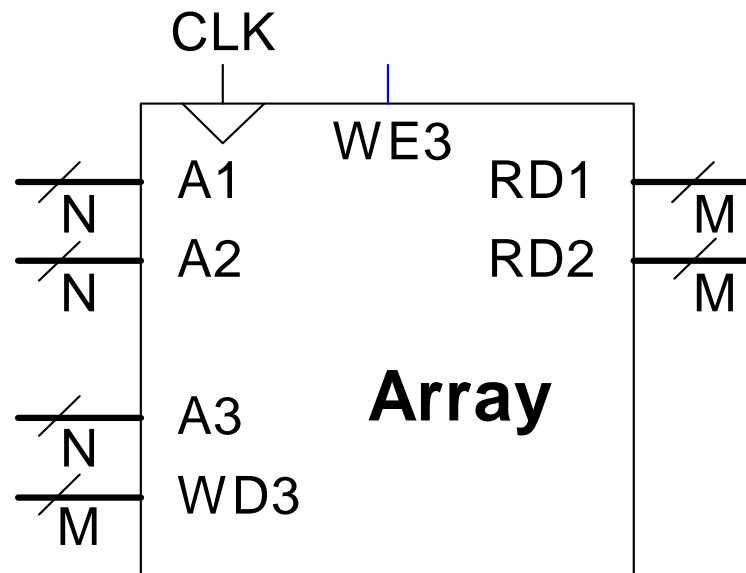- **Port:** address/data pair
- 3-ported memory
 - 2 read ports (A1/RD1, A2/RD2)
 - 1 write port (A3/WD3, WE3 enables writing)
- Small multi-ported memories are called *register files*



Verilog Memory Arrays

```
// 256 x 3 memory module with one read/write port
module dmem( input      clk, we,
             input  [7:0] a,
             input  [2:0] wd,
             output [2:0] rd);

    reg  [2:0] RAM[255:0];

    assign rd = RAM[a];



    always @(posedge clk)
        if (we)
            RAM[a] <= wd;
endmodule
```

Logic Arrays


- Programmable logic arrays (PLAs)
 - AND array followed by OR array
 - Perform combinational logic only
 - Fixed internal connections
- Field programmable gate arrays (FPGAs)
 - Array of configurable logic blocks (CLBs)
 - Perform combinational and sequential logic
 - Programmable internal connections

PLAs

 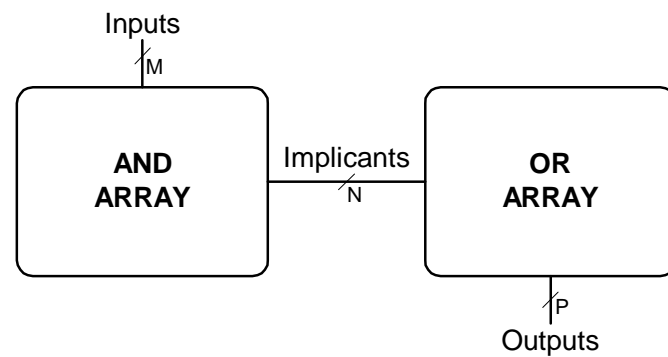- $X = \bar{A}\bar{B}C + A\bar{B}\bar{C}$
- $Y = A\bar{B}$




PLAs: Dot Notation

 

FPGAs: Field Programmable Gate Arrays

- Composed of:
 - **CLBs** (Configurable logic blocks): perform logic
 - **IOBs** (Input/output buffers): interface with outside world
 - **Programmable interconnection**: connect CLBs and IOBs
 - Some FPGAs include other building blocks such as multipliers and RAMs

Xilinx Spartan 3 FPGA Schematic

 


D8094-1_01_082703

CLBs: Configurable Logic Blocks

- Composed of:
 - LUTs (lookup tables): perform combinational logic
 - Flip-flops: perform sequential functions
 - Multiplexers: connect LUTs and flip-flops

Xilinx Spartan CLB

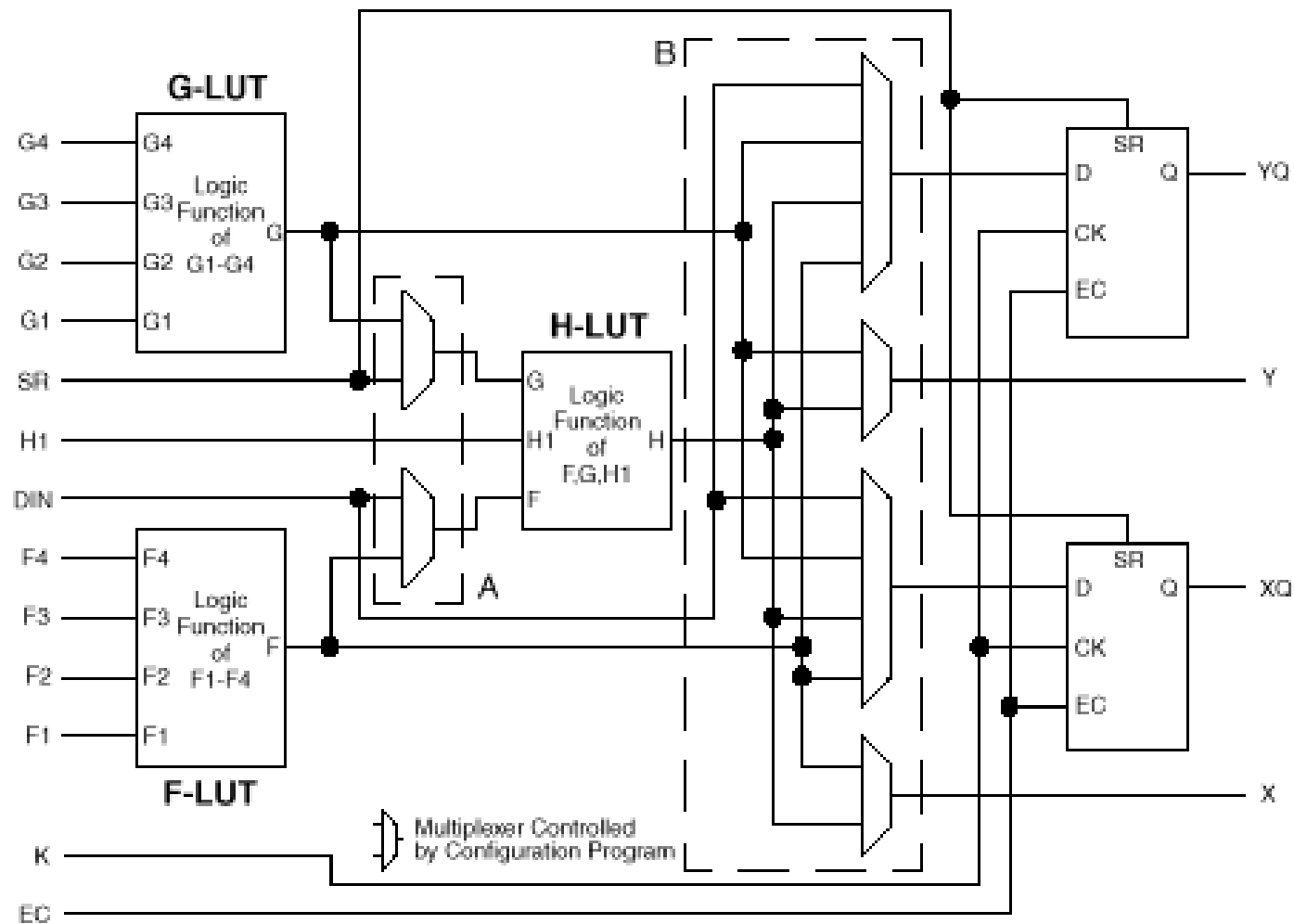


Xilinx Spartan CLB

- The Spartan CLB has:
 - 3 LUTs:
 - F-LUT ($2^4 \times 1$ -bit LUT)
 - G-LUT ($2^4 \times 1$ -bit LUT)
 - H-LUT ($2^3 \times 1$ -bit LUT)
 - 2 registered outputs:
 - XQ
 - YQ
 - 2 combinational outputs:
 - X
 - Y

CLB Configuration Example

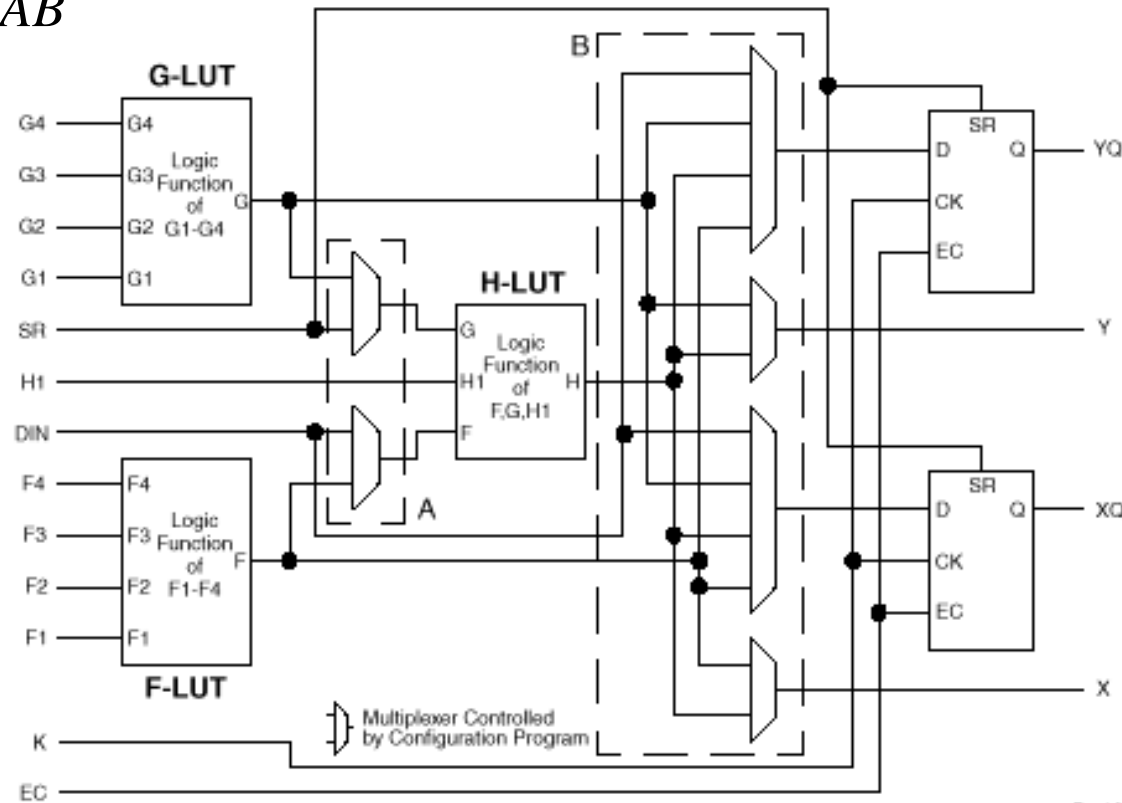- Show how to configure the Spartan CLB to perform the following functions:
 - $X = \overline{A}\overline{B}C + A\overline{B}C$
 - $Y = A\overline{B}$




CLB Configuration Example

- Show how to configure the Spartan CLB to perform the following functions:
 - $X = \overline{A}\overline{B}C + A\overline{B}\overline{C}$
 - $Y = A\overline{B}$

	(A)	(B)	(C)	(X)
F4	F3	F2	F1	F
X	0	0	0	0
X	0	0	1	1
X	0	1	0	0
X	0	1	1	0
X	1	0	0	0
X	1	0	1	0
X	1	1	0	1
x	1	1	1	0

		(A)	(B)	(Y)
G4	G3	G2	G1	G
X	X	0	0	0
X	X	0	1	0
X	X	1	0	1
X	X	1	1	0

 

FPGA Design Flow

- A CAD tool (such as Xilinx Project Navigator) is used to design and implement a digital system. It is usually an iterative process.
- The user **enters the design** using schematic entry or an HDL.
- The user **simulates** the design.
- A **synthesis** tool converts the code into hardware and maps it onto the FPGA.
- The user uses the CAD tool to **download the configuration** onto the FPGA
- This configures the CLBs and the connections between them and the IOBs.