


# Referat lucrare de laborator 2 – Constantinescu Vlad 314CB

## Exemplu 1

```
* C:\Users\Vlad\Desktop\Poli\ELTH\circuitT.cir
VPOLARIZARE 1 0 12
R1 1 2 10
R2 2 0 10
R3 2 3 5
R4 1 3 5
*
.OP
.END
```

--- Operating Point ---

V(1):	12	voltage
V(2):	8	voltage
V(3):	10	voltage
I(R4):	0.4	device_current
I(R3):	-0.4	device_current
I(R2):	0.8	device_current
I(R1):	0.4	device_current
I(Vpolarizare):	-0.8	device_current

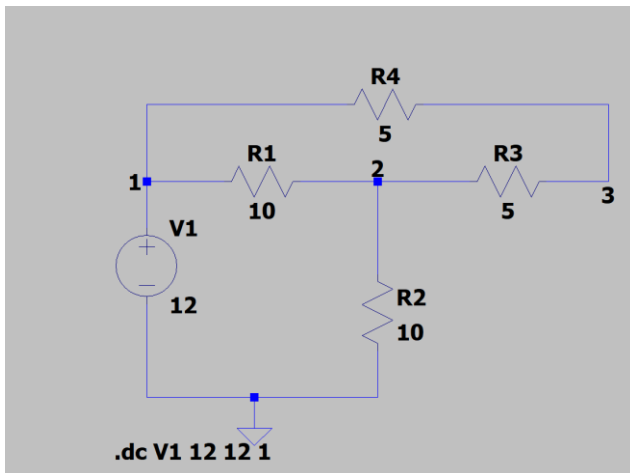

--- DC transfer characteristic ---


v1:	12	voltage
V(1):	12	voltage
V(2):	8	voltage
V(3):	10	voltage
I(R2):	0.8	device_current
I(R3):	0.4	device_current
I(R4):	-0.4	device_current
I(R1):	-0.4	device_current
I(V1):	-0.8	device_current

## Exemplu 2

```
* C:\Users\Vlad\Desktop\Poli\ELTH\cc1.cir
V1 2 0 90
V2 0 6 20
V3 4 5 20
I1 3 1 5
R1 1 6 20
R2 3 2 5
R3 1 4 10
R4 3 5 2
R5 5 0 5
.dc V1 90 90 1
.print dc I(R1) I(R2) I(R3) I(R4) I(R5) V(I1)
.end
```

--- DC transfer characteristic ---

v1:	90	voltage
I(R5):	6	device_current
I(R4):	5	device_current
I(R3):	1	device_current
I(R2):	-10	device_current
I(R1):	4	device_current

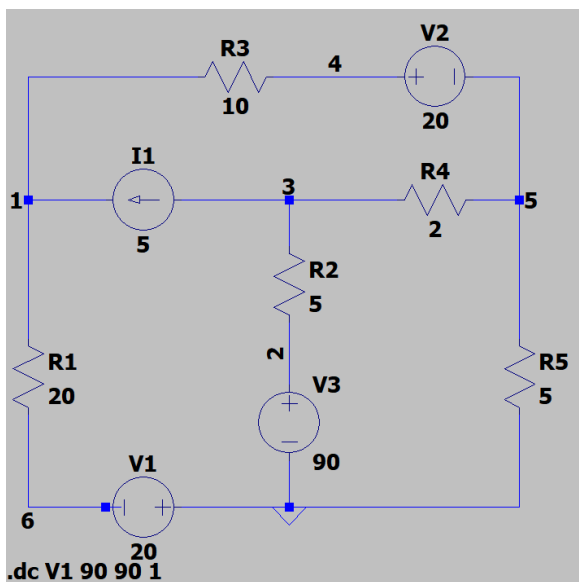

--- DC transfer characteristic ---

v1:	90	voltage
V(6):	-90	voltage
V(2):	90	voltage
V(1):	32.5316	voltage
V(4):	43.7975	voltage
V(5):	23.7975	voltage
V(3):	35.5696	voltage
I(I1):	5	device_current
I(R5):	4.75949	device_current
I(R2):	-10.8861	device_current
I(R3):	1.12658	device_current
I(R4):	-5.88608	device_current
I(R1):	6.12658	device_current
I(V2):	-1.12658	device_current
I(V3):	-10.8861	device_current
I(V1):	-6.12658	device_current

## Exercitiu 1


```
* C:\Users\Vlad\Desktop\Poli\ELTH\Lab2\Ex1\ex1.cir
```

```
V1 1 3 90
V2 4 3 50
V3 5 4 30
I1 1 0 6
R1 1 2 25
R2 0 3 12
R3 2 5 20
R4 3 2 10
R5 0 4 10
```

```
.dc V1 90 90 1
.print dc I(R1) I(R2) I(R3) I(R4) I(R5) V(I1)
.end
```

--- DC transfer characteristic ---
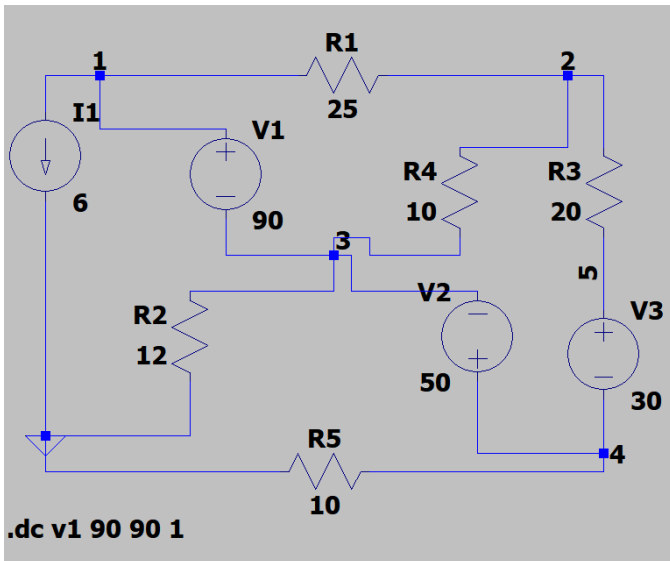
```
v1:          90          voltage
I(R5):        1          device_current
I(R4):       -4          device_current
I(R3):       -2          device_current
I(R2):        5          device_current
I(R1):        2          device_current
```



--- DC transfer characteristic ---

```
v1:          90          voltage
V(2):       -20          voltage
V(1):        30          voltage
V(3):       -60          voltage
V(5):        20          voltage
V(4):       -10          voltage
I(I1):        6          device_current
I(R5):        1          device_current
I(R4):       -4          device_current
I(R3):        2          device_current
I(R2):        5          device_current
I(R1):       -2          device_current
I(V3):       -2          device_current
I(V2):       -1          device_current
I(V1):       -8          device_current
```

## Exercitiu 2


```
* C:\Users\Vlad\Desktop\Poli\ELTH\Lab2\Ex2\ex2.cir
```

```
R1 3 4 1
R2 5 0 5
R4 2 1 4
R5 1 3 30
V1 3 5 115
V2 1 0 30
I1 4 2 10
R3 2 0 10
```

```
.dc v1 115 115 1
.print dc I(R1) I(R2) I(R3) I(R4) I(R5) V(I1)
.end
```

--- DC transfer characteristic ---
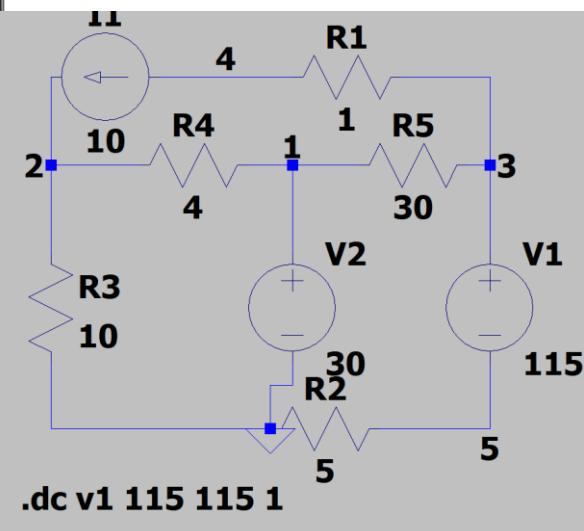
```
v1:          115         voltage
I(R3):        5          device_current
I(R5):       -1          device_current
I(R4):        5          device_current
I(R2):       -11         device_current
I(R1):       10          device_current
```



--- DC transfer characteristic ---

```
v1:          115         voltage
V(3):        60          voltage
V(4):        50          voltage
V(5):       -55          voltage
V(2):        50          voltage
V(1):        30          voltage
I(I1):       10          device_current
I(R3):        5          device_current
I(R5):       -1          device_current
I(R4):        5          device_current
I(R2):       -11         device_current
I(R1):       10          device_current
I(V2):        6          device_current
I(V1):      -11          device_current
```


### Exercitiul 3

```
* C:\Users\Vlad\Desktop\Poli\ELTH\Lab2\Ex3\ex3.cir
```

```
R1 2 4 20
R2 5 4 10
R3 2 1 20
R5 0 4 10
I1 3 2 6
V1 5 1 70
V2 1 0 10
R4 3 0 2
.dc v1 70 70 1
.print dc I(R1) I(R2) I(R3) I(R4) I(R5) V(I1)
.end
```

--- DC transfer characteristic ---

v1:	70	voltage
I(R4):	-6	device_current
I(R5):	-5	device_current
I(R3):	4	device_current
I(R2):	3	device_current
I(R1):	2	device_current

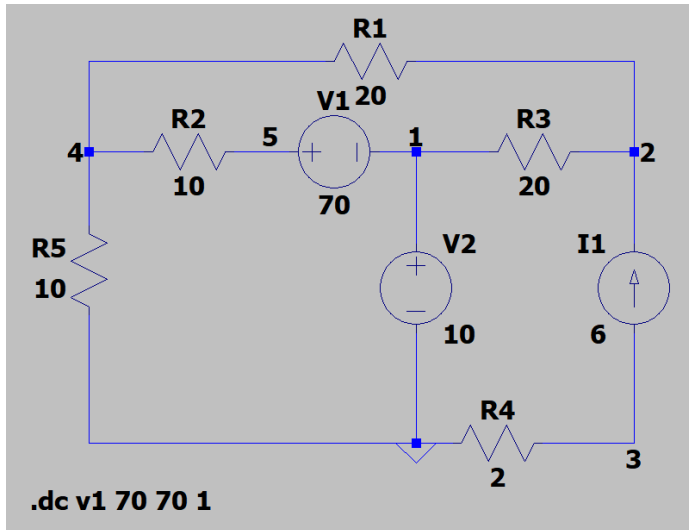

--- DC transfer characteristic ---

v1:	70	voltage
V(2):	90	voltage
V(4):	50	voltage
V(5):	80	voltage
V(1):	10	voltage
V(3):	-12	voltage
I(I1):	6	device_current
I(R4):	-6	device_current
I(R5):	-5	device_current
I(R3):	4	device_current
I(R2):	3	device_current
I(R1):	2	device_current
I(V2):	1	device_current
I(V1):	-3	device_current